

Design of Synchronous Sequential Logic

2016/12/12

范真璋

Ex1

實驗內容：

Exercise 1: Design of Sequence Detector (D-FF) (1/2)

- Design a sequence detector to detect a sequence of three or more consecutive 1's in a string of bits coming through an input line
 - ◆ The state diagram and state table of the sequence detector are shown in Fig. 5.27 and Table 5.11
 - ◆ Design the sequence detector with D flip-flops
 - ◆ Write the Verilog HDL description of the state diagram (i.e., **Behavioral model**)
 - ◆ Write the Verilog HDL description of the logic circuit diagram (i.e., a **Structural model**)
 - ◆ Write an Verilog HDL stimulus with a sequence of inputs: 0111110110. Verify that the responses are the same for both descriptions (first reset all flip-flops to 0).

Exercise 1: Design of Sequence Detector (D-FF) (2/2)

 


Table 5.11
State Table for Sequence Detector

Present State		Input <i>x</i>	Next State		Output <i>y</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Fig. 5.27 State diagram for sequence detector

程式碼：

(Behavioral model)


```
21 module ex1_state(  
22     output y_out,  
23     input x_in, clock, reset  
24 );  
25     reg [1: 0] state;  
26     parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;  
27     always @ (posedge clock, negedge reset)  
28     if (reset == 0) state <= S0; // Initialize to state S0  
29     else case (state)  
30     S0: if (x_in) state <= S1; else state <= S0;  
31     S1: if (x_in) state <= S2; else state <= S0;  
32     S2: if (x_in) state <= S3; else state <= S0;  
33     S3: if (x_in) state <= S3; else state <= S0;  
34     endcase  
35     assign y_out = (state == S3); // Output of flip-flops  
36  
37 endmodule
```

```
25 module ex1_state_tb;  
26  
27     // Inputs  
28     reg x_in;  
29     reg clock;  
30     reg reset;  
31  
32     // Outputs  
33     wire y_out;  
34  
35     // Instantiate the Unit Under Test (UUT)  
36     ex1_state uut (  
37         .y_out(y_out),  
38         .x_in(x_in),  
39         .clock(clock),  
40         .reset(reset)  
41     );  
42  
43     initial #200 $finish;  
44     initial begin clock = 0; forever #5 clock = ~clock; end  
45  
46     initial begin  
47         reset = 0;  
48         #2 reset = 1;  
49         #10 x_in = 0;  
50         #10 x_in = 1;  
51         #10 x_in = 1;  
52         #10 x_in = 1;  
53         #10 x_in = 1;  
54         #10 x_in = 1;  
55         #10 x_in = 0;  
56         #10 x_in = 1;  
57         #10 x_in = 1;  
58         #10 x_in = 0;  
59     end  
60  
61 endmodule
```

(Structural model)

```
21 module ex1_circuit(output y,A,B, input x,clock,reset);
22 wire t1,t2,t3,t4,t5;
23
24 and(t1,A,x);
25 and(t2,B,x);
26 or(t3,t1,t2);
27 d_flip_flop da(A,t3,clock,reset);
28 and(t4,~B,x);
29 and(y,B,A);
30 or(t5,t1,t4);
31 d_flip_flop db(B,t5,clock,reset);
32
33 endmodule
34
35 module d_flip_flop(output Q, input d,clk,reset);
36 wire t1,s,r,t2,q;
37
38 nand(t1,t2,s);
39 nand(s,t1,clk,reset);
40 nand(r,s,clk,t2);
41 nand(t2,r,d,reset);
42 nand(Q,s,q);
43 nand(q,Q,r,reset);
44
45 endmodule
46
47 module ex1_circuit_tb;
48
49 // Inputs
50 reg x;
51 reg clock;
52 reg reset;
53
54 // Outputs
55 wire y;
56 wire A;
57 wire B;
58
59 // Instantiate the Unit Under Test (UUT)
60 ex1_circuit uut (
61     .y(y),
62     .A(A),
63     .B(B),
64     .x(x),
65     .clock(clock),
66     .reset(reset)
67 );
68
69 initial #200 $finish;
70 initial begin clock = 0; forever #5 clock = ~clock; end
71
72 initial begin
73     reset = 0;
74     #2 reset = 1;
75     #10 x = 0;
76     #10 x = 1;
77     #10 x = 1;
78     #10 x = 1;
79     #10 x = 1;
80     #10 x = 1;
81     #10 x = 0;
82     #10 x = 1;
83     #10 x = 1;
84     #10 x = 0;
85 end
86
87 endmodule
```

實驗結果及分析：

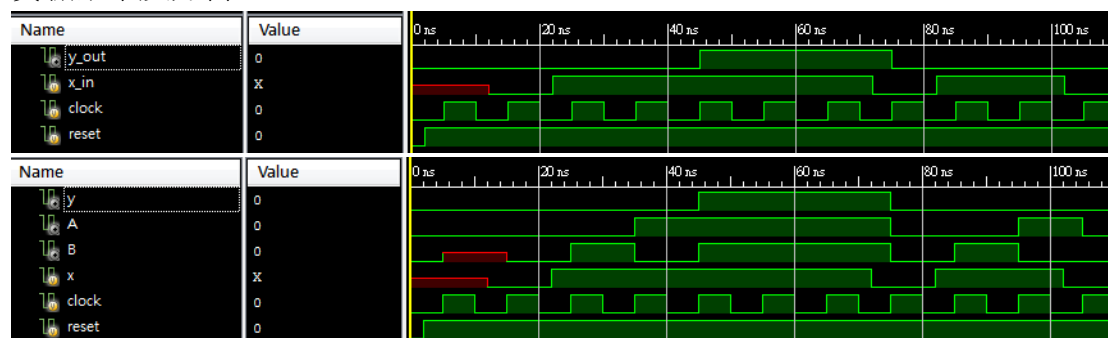

可以發現 output 只和 state 有關，為 Moore machine，且當有連續 3 個或以上的 1 時，output 為 1

Synthesis using D flip-flops

The flip-flop input (excitation) equations

- ◆ $A(t+1) = D_A(A, B, x) = \Sigma(3,5,7)$
- ◆ $B(t+1) = D_B(A, B, x) = \Sigma(1,5,7)$

The output equation

- ◆ $y(A, B, x) = \Sigma(6,7)$

Logic minimization using the K map

- ◆ $D_A = Ax + Bx$
- ◆ $D_B = Ax + B'x$
- ◆ $y = AB$

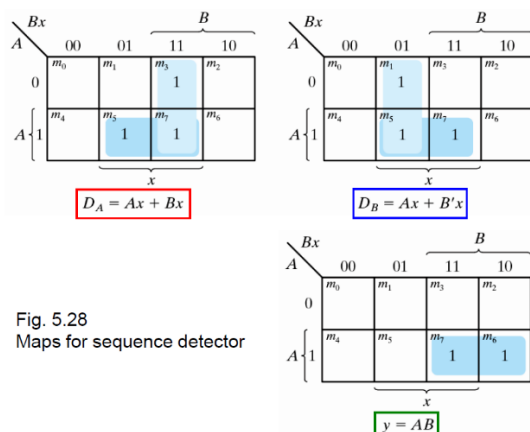


Fig. 5.28
Maps for sequence detector

Sequence detector

The logic diagram

$$\begin{aligned} D_A &= Ax + Bx \\ D_B &= Ax + B'x \\ y &= AB \end{aligned}$$

Table 5.11
State Table for Sequence Detector

Present State		Input		Next State		Output
A	B	x		A	B	y
0	0	0		0	0	0
0	0	1		0	1	0
0	1	0		0	0	0
0	1	1		1	0	0
1	0	0		0	0	0
1	0	1		1	1	0
1	1	0		0	0	1
1	1	1		1	1	1

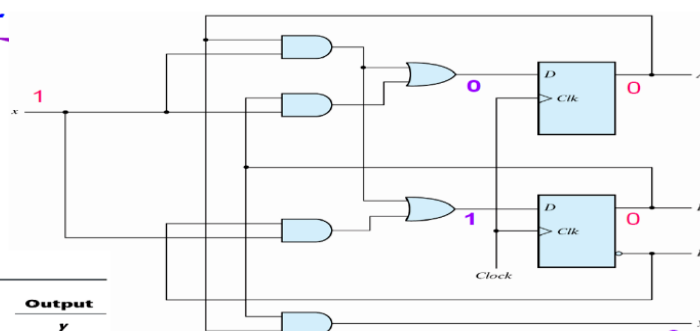


Fig. 5.29
Logic diagram of a Moore-type sequence detector

Ex2

實驗內容：

Exercise 2: Design of Sequence Detector (JK-FF)

- Design a sequence detector to detect a sequence of three or more consecutive 1's in a string of bits coming through an input line
 - ◆ The state diagram and state table of the sequence detector are shown in Fig. 5.27 and Table 5.11
 - ◆ Design the sequence detector with JK flip-flops
 - ◆ Write the Verilog HDL description of the state diagram (i.e., Behavioral model)
 - ◆ Write the Verilog HDL description of the logic circuit diagram (i.e., a Structural model)
 - ◆ Write an Verilog HDL stimulus with a sequence of inputs: 0111110110. Verify that the responses are the same for both descriptions (first reset all flip-flops to 0).

程式碼：

(Behavioral model)

同 Ex1

(Structural model)


```
21 module ex2_circuit(output y,A,B, input x,clock,reset);
22 wire t1,t2;
23
24 and(t1,x,B);
25 jk jka(A,t1,~x,clock,reset);
26 or(t2,~A,~x);
27 jk jkb(B,x,t2,clock,reset);
28 and(y,A,B);
29
30 endmodule
31
32 module jk(output Q, input j,k,clk,reset);
33 wire t1,s,r,t2,q,d,t3,t4;
34
35 and(t3,j,~Q);
36 and(t4,~k,Q);
37 or(d,t3,t4);
38 nand(t1,t2,s);
39 nand(s,t1,clk,reset);
40 nand(r,s,clk,t2);
41 nand(t2,r,d,reset);
42 nand(Q,s,q);
43 nand(q,Q,r,reset);
44
45 endmodule
```

```

25 module ex2_circuit_tb;
26
27     // Inputs
28     reg x;
29     reg clock;
30     reg reset;
31
32     // Outputs
33     wire A;
34     wire B;
35
36     // Instantiate the Unit Under Test (UUT)
37     ex2_circuit uut (
38         .y(y),
39         .A(A),
40         .B(B),
41         .x(x),
42         .clock(clock),
43         .reset(reset)
44     );
45
46     initial #200 $finish;
47     initial begin clock = 0; forever #5 clock = ~clock; end
48
49     initial begin
50         reset = 0;
51         #2 reset = 1;
52         #10 x = 0;
53         #10 x = 1;
54         #10 x = 1;
55         #10 x = 1;
56         #10 x = 1;
57         #10 x = 1;
58         #10 x = 0;
59         #10 x = 1;
60         #10 x = 1;
61         #10 x = 0;
62     end
63
64 endmodule

```

實驗結果及分析：

 

Synthesis using JK flip-flops

$Q(t)$	$Q(t + 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

State Table and JK Flip-Flop Inputs

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	0	0	0	X	X	1
0	1	1	1	0	1	X	X	1
1	0	0	0	0	X	1	0	X
1	0	1	1	1	X	0	1	X
1	1	0	0	0	X	1	X	1
1	1	1	1	1	X	0	X	0

$$J_A = Bx$$

$$K_A = x'$$

$$J_B = x$$

$$K_B = A' + x'$$

$$y = AB$$