

Three-state Gates, Latch, and D Flip-Flop

2016/11/28

范真璋

Ex1

實驗內容：

Exercise 1: 8-to-1 Multiplexer (1/2)


- Design and verify the 8-to-1 multiplexer composed of a 3×8 decoder and three-state gates using Verilog HDL

- ◆ Structural level (Gate-level) modeling

程式碼：

```
21 module Ex1(Y, s2, s1, s0, En, i0, i1, i2, i3, i4, i5, i6, i7);
22 output Y;
23 input s2, s1, s0, En, i0, i1, i2, i3, i4, i5, i6, i7;
24 wire d0, d1, d2, d3, d4, d5, d6, d7;
25 wire b0, b1, b2, b3, b4, b5, b6, b7;
26
27 and(d0, ~s2, ~s1, ~s0, En);
28 and(d1, ~s2, ~s1, s0, En);
29 and(d2, ~s2, s1, ~s0, En);
30 and(d3, ~s2, s1, s0, En);
31 and(d4, s2, ~s1, ~s0, En);
32 and(d5, s2, ~s1, s0, En);
33 and(d6, s2, s1, ~s0, En);
34 and(d7, s2, s1, s0, En);
35
36 bufif1(b0, i0, d0);
37 bufif1(b1, i1, d1);
38 bufif1(b2, i2, d2);
39 bufif1(b3, i3, d3);
40 bufif1(b4, i4, d4);
41 bufif1(b5, i5, d5);
42 bufif1(b6, i6, d6);
43 bufif1(b7, i7, d7);
44
45 or(Y, b0, b1, b2, b3, b4, b5, b6, b7);
46
47 endmodule
48
61 initial begin
62     // Initialize Inputs
63     s2 = 0; s1 = 0; s0 = 0; En = 0;
64     i0 = 1; i1 = 0; i2 = 0; i3 = 0; i4 = 0; i5 = 0; i6 = 0; i7 = 0;
65     #10
66     s2 = 0; s1 = 0; s0 = 0; En = 1;
67     i0 = 1; i1 = 0; i2 = 0; i3 = 0; i4 = 0; i5 = 0; i6 = 0; i7 = 0;
68     #10
69     s2 = 0; s1 = 0; s0 = 1; En = 1;
70     i0 = 0; i1 = 1; i2 = 0; i3 = 0; i4 = 0; i5 = 0; i6 = 0; i7 = 0;
71     #10
72     s2 = 0; s1 = 1; s0 = 0; En = 1;
73     i0 = 0; i1 = 0; i2 = 1; i3 = 0; i4 = 0; i5 = 0; i6 = 0; i7 = 0;
74     #10 $finish;
75 end
76 endmodule
77
```

實驗結果及分析：

 

s2	s1	s0	En	Y
X	X	X	0	X
0	0	0	1	i0
0	0	1	1	i1
0	1	0	1	i2

Ex2

實驗內容：

Exercise 2: D Latch

■ Design and verify the D latch using Verilog HDL

◆ Structural level (Gate-level) modeling

 


Fig. 5.6 D latch

(a) Logic diagram

程式碼：


```
21 module Ex2(Q1, Q2, D, En);
22   input D, En;
23   output Q1, Q2;
24   wire t1, t2;
25
26   nand(t1, D, En);
27   nand(t2, ~D, En);
28   nand(Q1, t1, Q2);
29   nand(Q2, Q1, t2);
30
31 endmodule
32
```

```

25 module Ex2_tb;
26
27     // Inputs
28     reg D;
29     reg En;
30
31     // Outputs
32     wire Q1;
33     wire Q2;
34
35     // Instantiate the Unit Under Test (UUT)
36     Ex2 uut (
37         .Q1(Q1),
38         .Q2(Q2),
39         .D(D),
40         .En(En)
41     );
42
43     initial begin
44         En = 0;
45         #10 D = 0;
46         #10 D = 1;
47         En = 1;
48         #10 D = 0;
49         #10 D = 1;
50         #10 $finish;
51     end
52 endmodule
53

```

實驗結果及分析：

 

En D		Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

Ex3

實驗內容：

Exercise 3: Master-slave D Flip-Flop

- Design and verify the positive-edge-triggered master-slave D flip-flop using Verilog HDL
 - ◆ Structural level (Gate-level) modeling

 


Fig. Positive-edge-triggered master-slave D flip-flop

程式碼：


```
21 module Ex3(Q1, Q2, C, D);
22   output Q1, Q2;
23   input C, D;
24
25   wire C1, C2, D1, D2;
26
27   not(C1, C);
28   not(C2, C1);
29   master m(D1, D2, D, C1);
30   slave s(Q1, Q2, C2, D1, D2);
31
32   endmodule
33
34   module master(mQ1, mQ2, mD, mEn);
35     input mD, mEn;
36     output mQ1, mQ2;
37     wire mt1, mt2;
38
39     nand(mt1, mD, mEn);
40     nand(mt2, ~mD, mEn);
41     nand(mQ1, mt1, mQ2);
42     nand(mQ2, mQ1, mt2);
43
44   endmodule
45
46   module slave(sQ1, sQ2, sEn, i1, i2);
47     input sEn, i1, i2;
48     output sQ1, sQ2;
49     wire st1, st2;
50
51     nand(st1, i1, sEn);
52     nand(st2, i2, sEn);
53     nand(sQ1, st1, sQ2);
54     nand(sQ2, sQ1, st2);
55
56   endmodule
57
```

```

25 module Ex3_tb;
26
27     // Inputs
28     reg C;
29     reg D;
30
31     // Outputs
32     wire Q1;
33     wire Q2;
34
35     // Instantiate the Unit Under Test (UUT)
36     Ex3 uut (
37         .Q1(Q1),
38         .Q2(Q2),
39         .C(C),
40         .D(D)
41     );
42
43     initial begin
44         C = 0;
45         #10 D = 0;
46         #10 D = 1;
47         C = 1;
48         #10 D = 0;
49         #10 D = 1;
50         #10 $finish;
51     end
52 endmodule
53

```

實驗結果及分析：

 

Clk	D	Q	Q'
↑	0	0	1

Ex4

實驗內容：

Exercise 4: D flip-flop with asynchronous reset

- Design and verify the D flip-flop with asynchronous reset shown in Fig. 5.14 using Verilog HDL (Gate-level modeling)

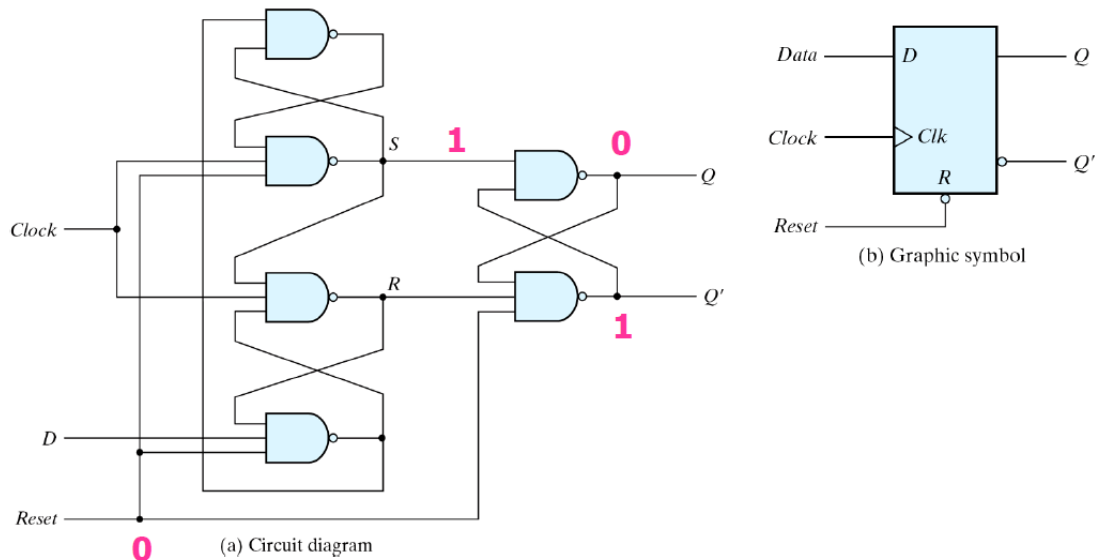


Fig. 5.14 D flip-flop with asynchronous reset

程式碼：


```
21 module Ex4(Q1, Q2, D, C, R);
22   output Q1, Q2;
23   input D, C, R;
24   wire t1, t2, t3, t4;
25
26   nand(t1, t2, D, R);
27   nand(t2, t3, C, t1);
28   nand(t3, t4, C, R);
29   nand(t4, t1, t3);
30   nand(Q1, t3, Q2);
31   nand(Q2, Q1, t2, R);
32
33 endmodule
34
```

```

25 module Ex4_tb;
26
27     // Inputs
28     reg D;
29     reg C;
30     reg R;
31
32     // Outputs
33     wire Q1;
34     wire Q2;
35
36     // Instantiate the Unit Under Test (UUT)
37     Ex4 uut (
38         .Q1(Q1),
39         .Q2(Q2),
40         .D(D),
41         .C(C),
42         .R(R)
43     );
44
45     initial #100 $finish;
46     initial begin C = 0; forever #5 C = ~C; end
47     initial fork
48         D = 1;
49         R = 1;
50         #20 D = 0;
51         #40 D = 1;
52         #50 D = 0;
53         #60 D = 1;
54         #70 D = 0;
55         #90 D = 1;
56         #42 R = 0;
57         #72 R = 1;
58     join
59 endmodule
60

```

實驗結果及分析：

 

R	Clk	D	Q	Q'
0	X	X	0	1
1	\uparrow	0	0	1
1	\uparrow	1	1	0