

Counter & Memory

2016/12/26

范真璋

Ex1

實驗內容：

Exercise 1: Four-bit up-down binary counter (1/2)

- Design and verify the four-bit up-down binary counter using T flip-flops with asynchronous reset and Verilog HDL
 - ◆ structural (gate-level) modeling

程式碼：


```
21 module ex1(output [3:0]a, input up,down,clk,rst);
22 wire t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11;
23
24 and(t1,~up,down);
25 or(t2,up,t1);
26
27 and(t3,t1,~a[0]);
28 and(t4,up,a[0]);
29 or(t5,t4,t3);
30
31 and(t6,t3,~a[1]);
32 and(t7,t4,a[1]);
33 or(t8,t6,t7);
34
35 and(t9,t6,~a[2]);
36 and(t10,t7,a[2]);
37 or(t11,t9,t10);
38
39 tff tff1(a[0],t2,clk,rst);
40 tff tff2(a[1],t5,clk,rst);
41 tff tff3(a[2],t8,clk,rst);
42 tff tff4(a[3],t11,clk,rst);
43
44 endmodule
45
46 module tff(output Q, input t,clk,reset);
47 wire t1,s,r,t2,q,d;
48
49 xor(d,Q,t);
50 nand(t1,t2,s);
51 nand(s,t1,clk,reset);
52 nand(r,s,clk,t2);
53 nand(t2,r,d,reset);
54 nand(Q,s,q);
55 nand(q,Q,r,reset);
56
57 endmodule
```

```

25 module ex1_tb;
26
27     // Inputs
28     reg up;
29     reg down;
30     reg clk;
31     reg rst;
32
33     // Outputs
34     wire [3:0] a;
35
36     // Instantiate the Unit Under Test (UUT)
37     ex1 uut (
38         .a(a),
39         .up(up),
40         .down(down),
41         .clk(clk),
42         .rst(rst)
43     );
44
45     initial begin clk = 0; forever #5 clk = ~clk; end
46     initial begin
47         rst = 0;
48         up = 0;
49         down = 1;
50         #10 rst = 1;
51         #10 down = 1;
52         #10 down = 1;
53         #10 down = 1;
54         #10 down = 1;
55         #10 down = 1;
56         #10 down = 0; up = 1;
57         #10 down = 0; up = 1;
58         #10 down = 0; up = 1;
59         #10 down = 0; up = 1;
60         #10 down = 0; up = 1;
61         #10 down = 0; up = 1;
62         #10 down = 1;
63
64     end
65     initial #200 $finish;
66 endmodule

```

實驗結果及分析：

 

Up	Down	Function
0	0	No Change
0	1	Down
1	0	Up
1	1	Up

一開始 reset 為 0，之後從 1111 開始減 5 次變成 1010(up=0,down=1)，然後再加 6 次變成 0000(up=1,down=0)，後面因為 up 和 down 同時為 1，所以一直加到結束

Ex2

實驗內容：

Exercise 2: 4 x 4 RAM (1/2)

■ Design and verify the 4 x 4 RAM using Verilog HDL

◆ Structural modeling

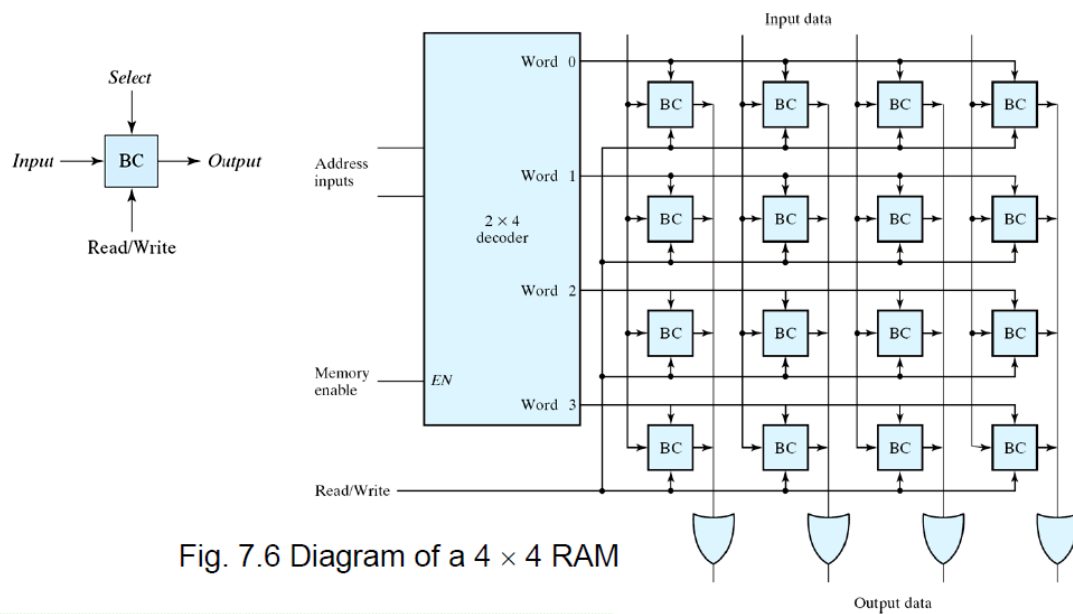


Fig. 7.6 Diagram of a 4 x 4 RAM

程式碼：

```

21 module EX2(output [3:0]o, input mem,rw,input[3:0]i,input[1:0]a);
22 wire [3:0]d;
23 wire [15:0]t;
24
25 decoder_case twotofour(a, d , mem);
26
27 bc bc1 (t[0],i[0],d[0],rw);
28 bc bc2 (t[1],i[0],d[1],rw);
29 bc bc3 (t[2],i[0],d[2],rw);
30 bc bc4 (t[3],i[0],d[3],rw);
31 or (o[0],t[0],t[1],t[2],t[3]);
32
33 bc bc5 (t[4],i[1],d[0],rw);
34 bc bc6 (t[5],i[1],d[1],rw);
35 bc bc7 (t[6],i[1],d[2],rw);
36 bc bc8 (t[7],i[1],d[3],rw);
37 or (o[1],t[4],t[5],t[6],t[7]);
38
39 bc bc9 (t[8],i[2],d[0],rw);
40 bc bc10 (t[9],i[2],d[1],rw);
41 bc bc11 (t[10],i[2],d[2],rw);
42 bc bc12 (t[11],i[2],d[3],rw);
43 or (o[2],t[8],t[9],t[10],t[11]);
44
45 bc bc13 (t[12],i[3],d[0],rw);
46 bc bc14 (t[13],i[3],d[1],rw);
47 bc bc15 (t[14],i[3],d[2],rw);
48 bc bc16 (t[15],i[3],d[3],rw);
49 or (o[3],t[12],t[13],t[14],t[15]);
50
51 endmodule


```

```

53 module decoder_case(binary_in, decoder_out , enable);
54     input [1:0] binary_in ; // 2 bit binary input
55     input enable ; // Enable for the decoder
56     output [3:0] decoder_out ; // 4-bit out
57
58     reg [3:0] decoder_out ;
59
60     always @ (enable or binary_in)
61     begin
62         decoder_out = 0;
63         if (enable) begin
64             case (binary_in)
65                 2'b00 : decoder_out = 4'b0001;
66                 2'b01 : decoder_out = 4'b0010;
67                 2'b10 : decoder_out = 4'b0100;
68                 2'b11 : decoder_out = 4'b1000;
69             endcase
70         end
71     end
72 endmodule
73
74 module bc(output o, input i,s,rw);
75     reg q,o;
76
77     always @ (i or s or rw)
78     if(s)
79         if(rw) o=q;
80         else q=i;
81     else o=0;
82 endmodule
83
25 module ex2_tb;
26
27     // Inputs
28     reg mem;
29     reg rw;
30     reg [3:0] i;
31     reg [1:0] a;
32
33     // Outputs
34     wire [3:0] o;
35
36     // Instantiate the Unit Under Test (UUT)
37     EX2 uut (
38         .o(o),
39         .mem(mem),
40         .rw(rw),
41         .i(i),
42         .a(a)
43     );
44     initial #150 $finish;
45
46     initial begin
47         mem = 1;
48         rw = 0;
49         a = 0;
50         i = 0;
51         #10 rw=1'b0;
52         #10 a=2'b00;#1 i=4'b0001;
53         #10 a=2'b01;#1 i=4'b0010;
54         #10 a=2'b10;#1 i=4'b0011;
55         #10 a=2'b11;#1 i=4'b0100;
56         #10 a=2'bxx;#1 i=4'bxxxx;
57         #10 rw=1'b1;
58         #10 a=2'b00;
59         #10 a=2'b01;
60         #10 a=2'b10;
61         #10 a=2'b11;
62     end
63 endmodule

```

實驗結果及分析：

 

前半部 rw=0 為 write 操作，將 input 寫入記憶元件中；後半部 rw=1 為 read 操作，讀取前面儲存的資料；當 address(a)為 00，經過 decoder 後，第一列的 BC 做寫入或讀取