

# Karnaugh Map & Don't-Care Conditions

2016/10/24

范真璋

Ex1

實驗內容：

## Exercise 1

- Simplify the Boolean function  $F(w,x,y,z) = \Sigma (0,1,2,5,8,9,10)$  using Karnaugh maps to (1) **the simplest sum of products (F1)**, and (2) **the simplest product of sums (F2)**
- Verify  $F1 = F2$  (using Verilog Dataflow modeling)

程式碼：

```
module Ex1(F1, F2, w, x, y, z);
output F1, F2;
input w, x, y, z;

wire F1, F2, w, x, y, z;

assign F1 = ~x&~z | ~x&~y | ~w&~y&z;
assign F2 = (~y|~z) & (~w|~x) & (~x|z);

endmodule

module Ex1_tb;
reg w;
reg x;
reg y;
reg z;

// Outputs
wire F1;
wire F2;

// Instantiate the Unit Under Test (UUT)
Ex1 uut (
.w(w),
.x(x),
.y(y),
.z(z),
.F1(F1),
.F2(F2)
);

initial begin
// Initialize Inputs
w=0;x=0;y=0;z=0;
#10 w=0;x=0;y=0;z=1;
#10 w=0;x=0;y=1;z=0;
#10 w=0;x=0;y=1;z=1;
#10 w=0;x=1;y=0;z=0;
#10 w=0;x=1;y=0;z=1;
#10 w=0;x=1;y=1;z=0;
#10 w=0;x=1;y=1;z=1;
#10 w=1;x=0;y=0;z=0;
#10 w=1;x=0;y=0;z=1;
#10 w=1;x=0;y=1;z=0;
#10 w=1;x=0;y=1;z=1;
#10 w=1;x=1;y=0;z=0;
#10 w=1;x=1;y=0;z=1;
#10 w=1;x=1;y=1;z=0;
#10 w=1;x=1;y=1;z=1;
#10 $finish;


end
endmodule
```

實驗結果及分析：

	00	01	11	10
00	1	1		1
01		1		
11				
10	1	1		1

$$F1 = \sim x \& \sim z \mid \sim x \& \sim y \mid \sim w \& \sim y \& z$$
 
$$F2 = (\sim y \& \sim z) \& (\sim w \mid \sim x) \& (\sim x \& z)$$



由實驗結果圖中的波形得知  $F1 = F2$

## Ex2

實驗內容：

### Exercise 2

- Simplify the following Boolean function using Karnaugh maps:  
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$
- Find the simplest sum of products ( $F1$ ) and draw its logic diagram (two-level implementation)
  - ◆ Implement  $F1$  with two-level NAND gate circuit (denoted as  $F2$ )
  - ◆ Verify  $F1 = F2$  (using Verilog Structural level modeling)
- Find the simplest product of sums ( $F3$ ) and draw its logic diagram (two-level implementation)
  - ◆ Implement  $F3$  with two-level NOR gate circuit (denoted as  $F4$ )
  - ◆ Verify  $F3 = F4$  (using Verilog Structural level modeling)

程式碼：

```
module Ex2(F1, F2, F3, F4, x, y, z);
output F1, F2, F3, F4;
input x, y, z;

wire F1, F2, F3, F4, x, y, z, t1, t2, t3, t4;

assign F1 = z | x&~y | ~x&y;
nand(t1, x, ~y);
nand(t2, ~x, y);
nand(F2, ~z, t1, t2);

assign F3 = (x|y|z) & (~x|~y|z);
nor(t3, x, y, z);
nor(t4, ~x, ~y, z);
nor(F4, t3, t4);

endmodule

module Ex2_tb;

    // Inputs
    reg x;
    reg y;
    reg z;

    // Outputs
    wire F1;
    wire F2;
    wire F3;
    wire F4;

    // Instantiate the Unit Under Test (UUT)
    Ex2 uut (
        .F1(F1),
        .F2(F2),
        .F3(F3),
        .F4(F4),
        .x(x),
        .y(y),
        .z(z)
    );


    initial begin
        // Initialize Inputs
        x = 0; y = 0; z = 0;
        #10 x = 0; y = 0; z = 1;
        #10 x = 0; y = 1; z = 0;
        #10 x = 0; y = 1; z = 1;
        #10 x = 1; y = 0; z = 0;
        #10 x = 1; y = 0; z = 1;
        #10 x = 1; y = 1; z = 0;
        #10 x = 1; y = 1; z = 1;
        #10 $finish;
    end
endmodule
```

實驗結果及分析：

	00	01	11	10
0		1	1	1
1	1	1	1	

$$F1 = z \mid x \& \sim y \mid \sim x \& y$$
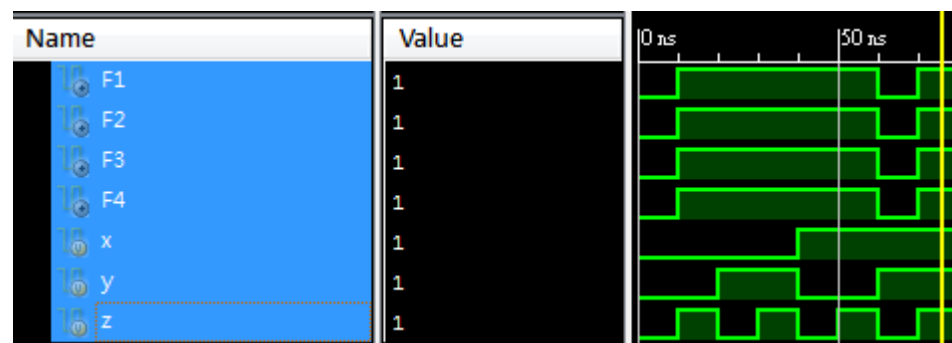
$$F3 = (x \mid y \mid z) \& (\sim x \mid \sim y \mid \sim z)$$




由實驗結果圖中的波形得知  $F1 = F2$ ， $F3 = F4$ ，且  $F1 = F2 = F3 = F4$

Ex3


實驗內容：
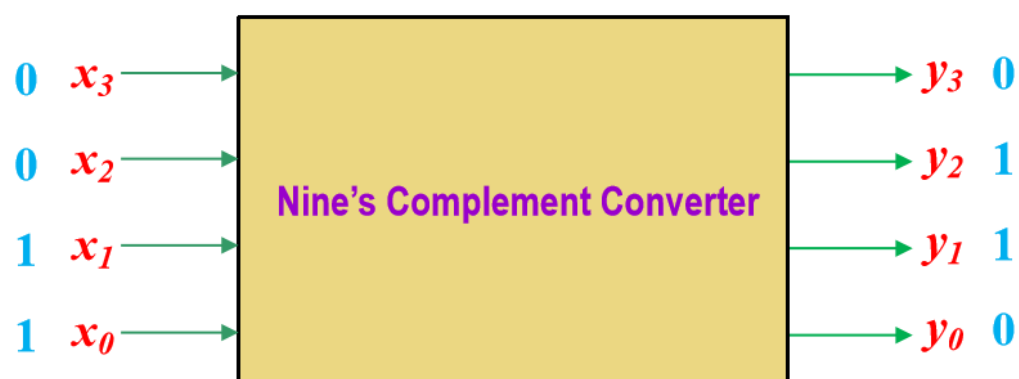
### Exercise 3: Nine's Complement Converter (2/2)

- Design the nine's complement converter using Karnaugh maps and don't-care conditions, draw the **logic diagram** of the nine's complement converter and verify the circuit (using Schematic)



電路圖：

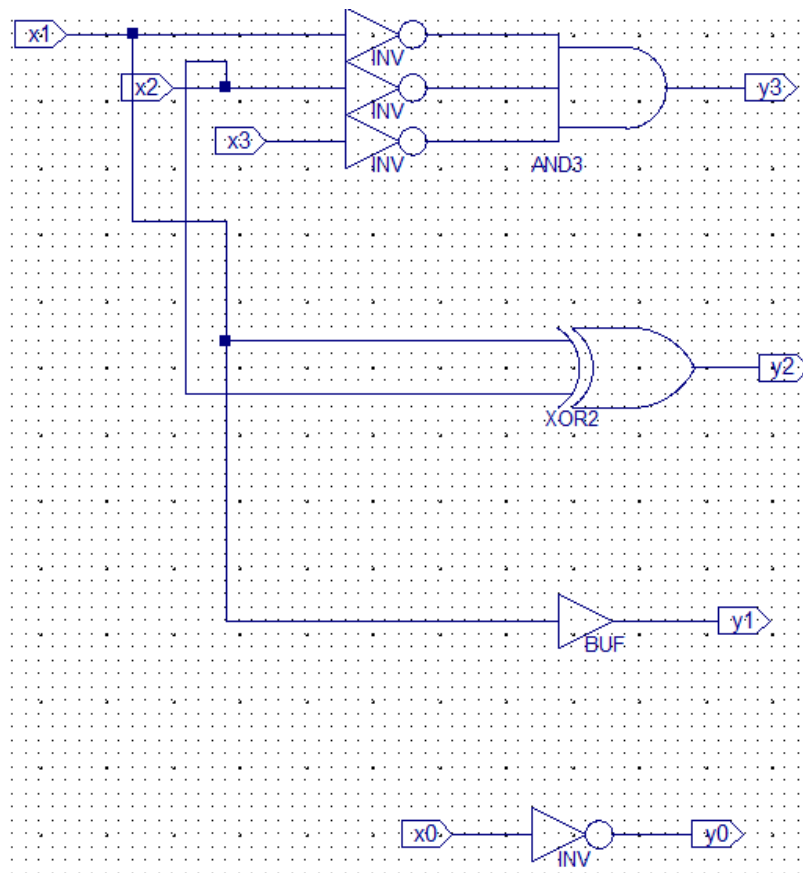

程式碼：

```
module Ex3_Ex3_sch_tb();

// Inputs
reg x3;
reg x0;
reg x1;
reg x2;

// Output
wire y3;
wire y2;
wire y0;
wire y1;


// Bidirs

// Instantiate the UUT
Ex3 UUT (
    .x3(x3),
    .x0(x0),
    .y3(y3),
    .y2(y2),
    .y0(y0),
    .x1(x1),
    .y1(y1),
    .x2(x2)
);

// Initialize Inputs
initial begin
    x3=0; x2=0; x1=0; x0=0;
    #10 x3=0; x2=0; x1=0; x0=1;
    #10 x3=0; x2=0; x1=1; x0=0;
    #10 x3=0; x2=0; x1=1; x0=1;
    #10 x3=0; x2=1; x1=0; x0=0;
    #10 x3=0; x2=1; x1=0; x0=1;
    #10 x3=0; x2=1; x1=1; x0=0;
    #10 x3=0; x2=1; x1=1; x0=1;
    #10 x3=1; x2=0; x1=0; x0=0;
    #10 x3=1; x2=0; x1=0; x0=1;
    #10 $finish;
end

endmodule
```

實驗結果及分析：

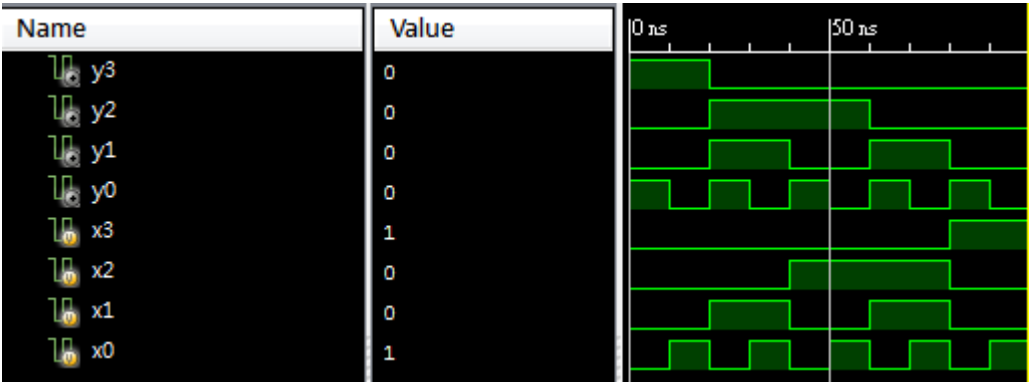

Digits		Nine's Complements	
Decimal	BCD	Decimal	BCD
$x_3x_2x_1x_0$		$y_3y_2y_1y_0$	
0	0000	9	1001
1	0001	8	1000
2	0010	7	0111
3	0011	6	0110
4	0100	5	0101
5	0101	4	0100
6	0110	3	0011
7	0111	2	0010
8	1000	1	0001
9	1001	0	0000

Nine's-complement table

$x_1, x_2$	$x_3, x_0$			
	00	01	11	10
00	1	1		
01				
11	X	X	X	X
10			X	X

$$y_3 = x_3'x_2'x_1'$$

$x_1, x_2$	$x_3, x_0$			
	00	01	11	10
00			1	1
01	1	1		
11	X	X	X	X
10			X	X

$$y_2 = x_2 \oplus x_1$$

$x_1, x_2$	$x_3, x_0$			
	00	01	11	10
00			1	1
01			1	1
11	X	X	X	X
10			X	X

$$y_1 = x_1$$

$x_1, x_2$	$x_3, x_0$			
	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X

$$y_0 = x_0'$$

電路圖依據此圖完成九補數轉換器，兩數相加為  $9_{10}=(1001)_2$